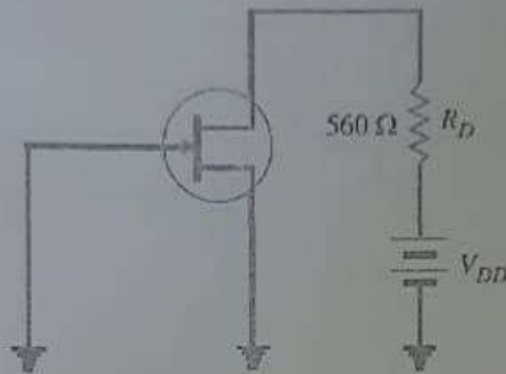


- Q4 (a) What are the types of possible configurations in BJT. Derive the relation between β_o , β and γ . $\beta_o = \beta \gamma$ [3] CO2 BL1
- Q4 (b) In a fixed biased circuit of CE-transistor, $V_{CC} = 15\text{ V}$, $R_B = 820\text{ K}\Omega$, $R_C = 4.7\text{ K}\Omega$, $V_{BE} = 0.7\text{ V}$ and $\beta = 120$. Draw the DC load line and locate the operating point. [2] CO2 BL4
- Q5 (a) With a neat sketch, explain the operation of n-channel enhancement type MOSFET. [3] CO2 BL2
- Q5 (b) For the JFET in Figure, $V_{GS}(\text{off}) = -4\text{ V}$ and $I_{DSS} = 12\text{ mA}$. Determine the minimum value of V_{DD} required to put the device in the constant-current region of operation. [2] CO2 BL2



BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI
(MID SEMESTER EXAMINATION)

CLASS: BTECH
BRANCH: CSE/ECE/EEE/AI & ML

SEMESTER: I
SESSION: MO/2022

SUBJECT: EC101 BASICS OF ELECTRONICS AND COMMUNICATION ENGINEERING

TIME: 2 HOURS

FULL MARKS: 25

INSTRUCTIONS:

1. The question paper contains 5 questions each of 5 marks and total 25 marks.
2. Attempt all questions.
3. The missing data, if any, may be assumed suitably.
4. Tables/Data handbook/Graph paper etc., if applicable, will be supplied to the candidates

- Q1 (a) Describe the operation of Zener Diode based voltage regulator with a suitable circuit diagram. [3] CO1 BL2
- Q1 (b) In the following Fig.1, If Germanium (Ge) diode connection (direction) is reversed, the value of output voltage (V_o) changes by how much volts? [2] CO1 BL4
(Assume that the Ge diode has large breakdown voltage).

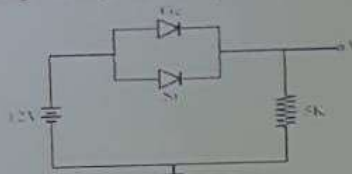


Fig. 1

- Q2 (a) Draw the circuit of diode based Half Wave Rectifier (HWR) and Derive the expressions for average and RMS voltage for HWR. [3] CO1 BL1
- Q2 (b) A full wave rectifier produces a rms voltage of 10 V from a 50 Hz line source and feeds a resistive load of 1100 Ω . If the filter uses a capacitor of $C = 50 \mu\text{F}$, calculate the output dc voltage and ripple voltage. [2] CO1 BL4
- Q3 (a) Explain Base-width Modulation Effect in BJT using suitable diagram. [3] CO2 BL2
- Q3 (b) Find the Quiescent-point voltage and current values for voltage divider configuration shown (Fig2) [2] CO2 BL4

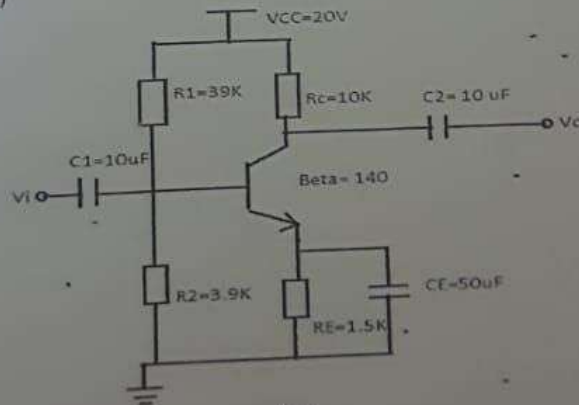


Fig2

PTO